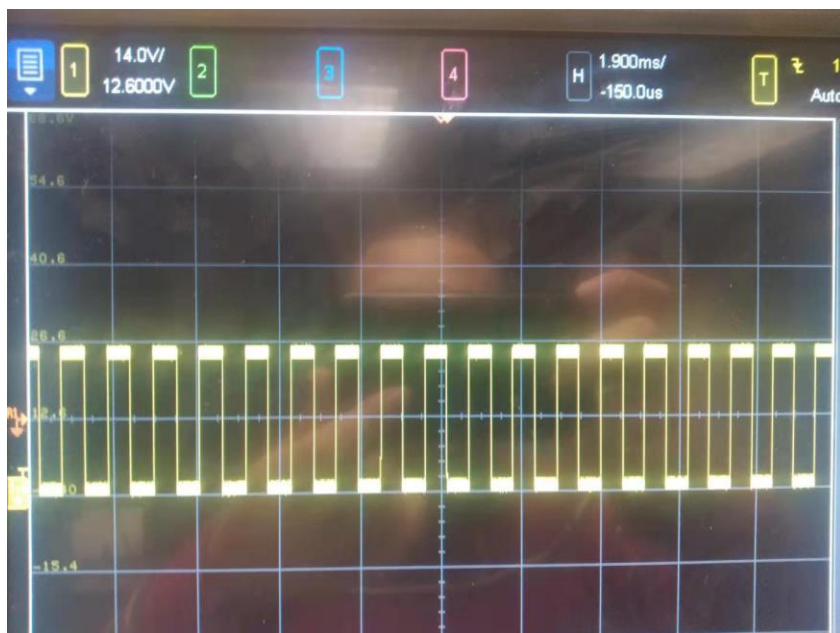


The oscillator circuit with 7414 an inverter as buffer.



The oscillating result, the crystal is oscillating at 16mhz.