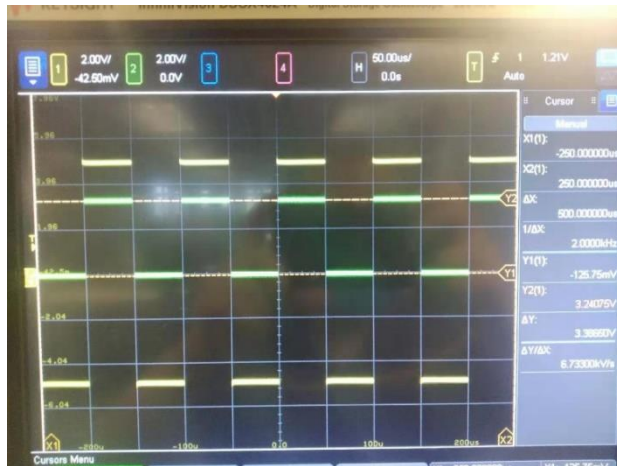


1. Measure from channel 1 and channel 2 when channel 1 is connected function generator and channel 2 is connected to sync signal.

Below is the figure measured from sync signal and function generator. When the scope is triggered by sync signal, the function generator is outputting the 10V p-p square wave of 10kHz at rising time.

It is expected to see from channel 1 a 10V p-p square wave of 10kHz square wave. It measures the square wave function generator generated.

It is expected to see from channel 2 the sync signal generated. It measures the sync signal synchronous the square wave with TTL level of 3.3 volts.





2. Rise time and fall time of the signal.



It gives 10ns of rise time 10ns of fall time.

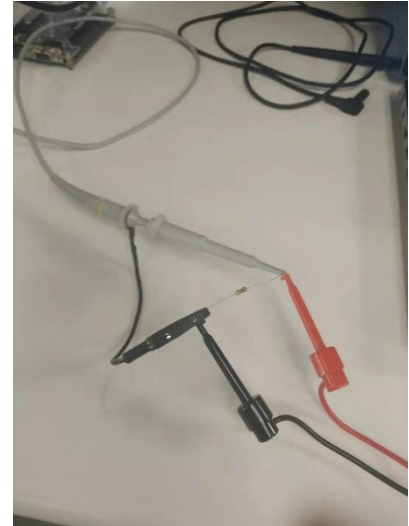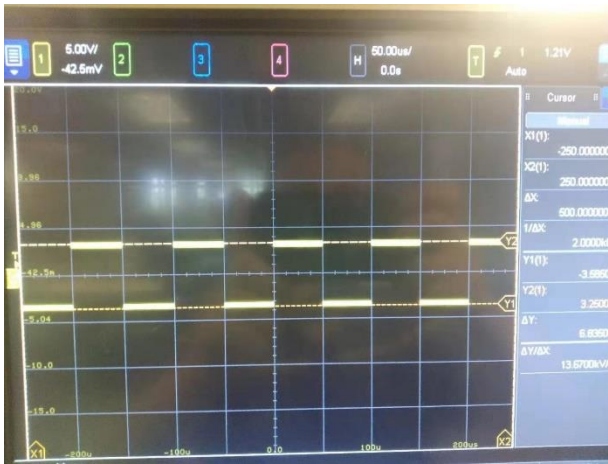3. Thevenin output voltage measured with load 100ohm



It gives Thevenin output voltage of  $V_{thevenin_{output}} = 3.25$   $V_{output} = 4.96v$   $R_{load} = 100ohm$

$$(V_{output} - V_{thevenin_{output}})/V_{thevenin_{output}} = R_{thevenin_{res}}/R_{load}$$

$$R_{thevenin_{res}} = 52.6ohm$$

The Thevenin resistor is approximately equal to 50ohm.

When the function generator output load to be 50 ohms, because the load resistance is limited with 100ohm other than required 50 ohms. When connected with load resistor, p-p voltage measured from scope is 6.66v but it expected as 5v (instead of 10v) read from the generator. This model does not change the Thevenin resistance, it is still measured approximately 50ohm.

4. Inductively coupled cross talk between victim loop and aggressor loop

$$dI/dt: \text{ It has positive current of } 100mA \text{ with } 5v \text{ and } -100mA \text{ with } -5v. \frac{dI}{dt} = \frac{200mA}{10ns} = 20mA/ns$$

Current direction: When the signal is rising, the current direction of at first is negative (from ground to output) the signal level rise to 0. When the signal level rise above zero, the current direction becomes positive (from output to ground).

Mutual inductance: the figure below is the aggressor on top of the victim loop with same Direction and the figure of flipping of the aggressor loop.


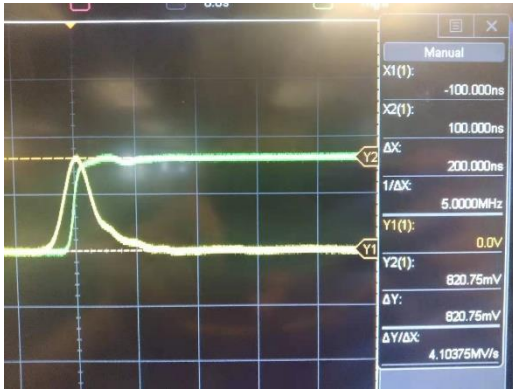


Figure of aggressor and victim of same direction,  
The signature of noise is positive.  
Flipping the direction of aggressor loop, the signature of the noise also got flipped.

Figure of aggressor and victim of different  
Direction, the signature is negative.


Decoupling noise with different aggressor and victim geometries.

Large loops far apart:

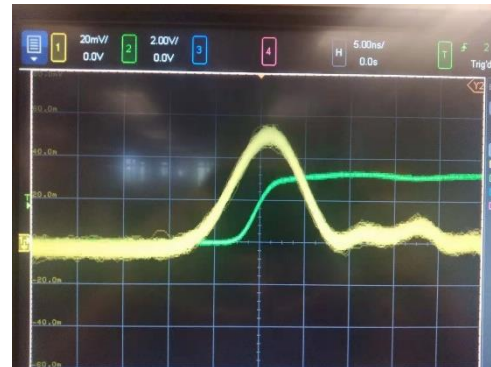



(The noise have same direction because the loops have same direction)

Large loops overlapping

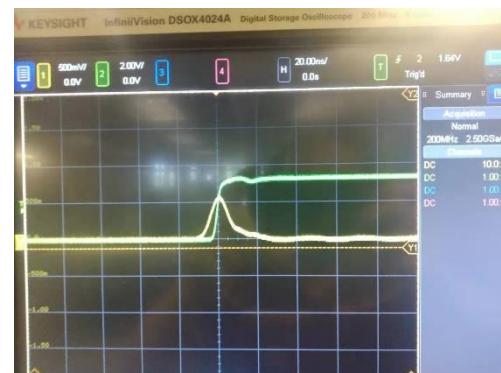


(Put two loops closer, the noise gets larger)

Large loops overlapping returns

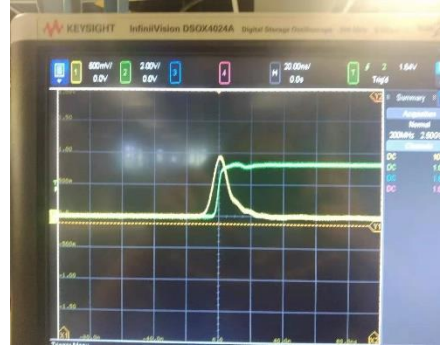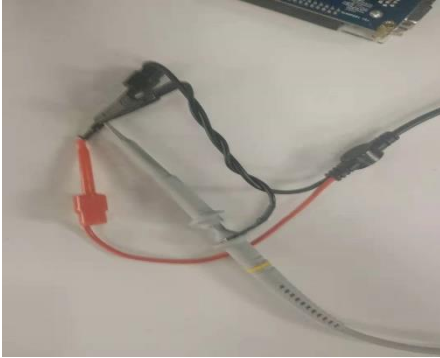

(Put two loops further close, the noise gets larger)

Small loops far apart

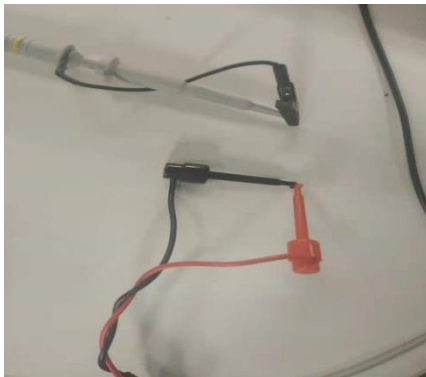

(Reduce the size of the loop and makes them apart, the noise get reduced by a lot)

The design guideline to reduce synchronous noise is to make the loop as small as possible and make them as far apart as possible.