

1. Comparison of switching noise of good and bad layout
 - (1) The quiet high output of good layout, p-p 132mV




- (2) The quiet low output of good layout, p-p 56.3mV



(3) The quiet high output of bad layout, p-p 678mV



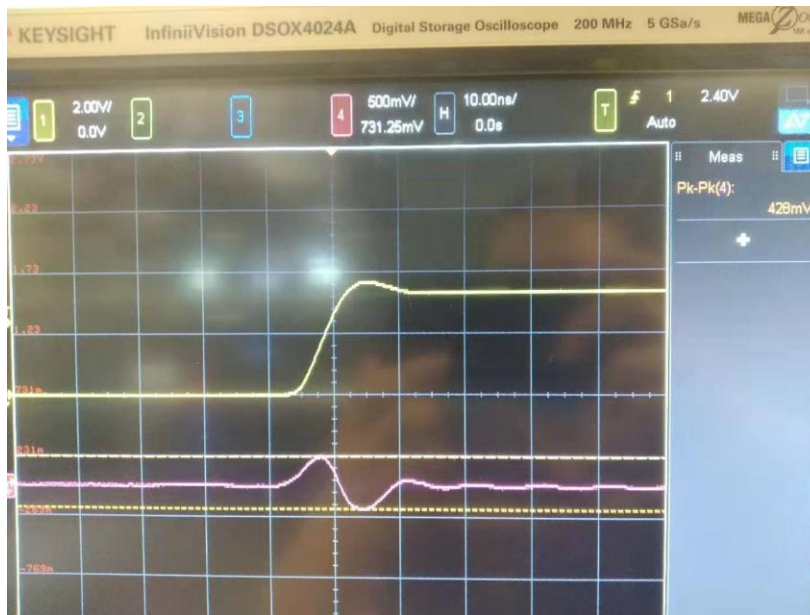(4) The quiet low output of bad layout, p-p 428mV



From the traces above, it tells that the bad layout adds the great amount of noise.

There are three contributing factors:

- (1) The good layout has a return plane, but the bad doesn't.
- (2) The good has the decoupling cap near the IC, but the bad one has it far away.
- (3) The signal traces of the good one is connected short with small loop inductance, while the bad one has very long wires.